

## Introduction to Bioelectricity Part I

ENGR 1166 Biomedical Engineering

---

---

---

---

---

---

---

---

### What is "bioelectricity"?



- It studies the electric phenomena produced by or occurring within living organisms

---

---

---

---

---

---


---

---
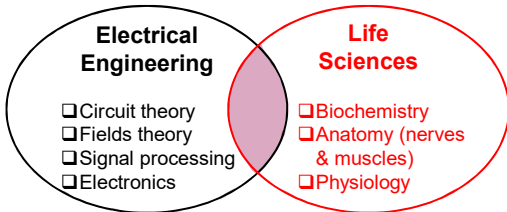
### What is "bioelectricity"?



- It studies the electric phenomena produced by or occurring within living organisms
- It combines Engineering and Life Sciences



---

---

---

---

---

---

---

---

## Bioelectricity: areas of interest



Bioelectricity

---

---

---

---

---

---

---

---

## Bioelectricity: areas of interest



Bioelectricity

To measure the electric signals produced by the activity of living tissues

---

---

---

---

---

---

---

---


## Bioelectricity: areas of interest



Bioelectricity

To measure the electric signals produced by the activity of living tissues

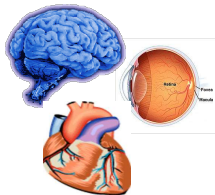- Electroencephalography (EEG)
- Electroretinography (ERG)
- Electrocardiography (ECG)
- electromyography (EMG)



---

---

---

---


---

---

---

---

**Bioelectricity: areas of interest**



```
graph TD; A[Bioelectricity] --> B[To measure the electric signals produced by the activity of living tissues]; A --> C[To study the effect of electric fields due to an external device on tissue]
```

To measure the electric signals produced by the activity of living tissues

To study the effect of electric fields due to an external device on tissue

---

---

---

---


---

---

---

---

**Bioelectricity: areas of interest**



```
graph TD; A[Bioelectricity] --> B[To measure signals]; A --> C[To study the effect of electric fields due to an external device on tissue]; B --- D[Images: Brain scan, leg with device, heart with defibrillator]; C --- E[Deep brain stimulation (DBS), Functional stimulation (FES), Cardiac defibrillation (CDF)]
```

To measure signals

To study the effect of electric fields due to an external device on tissue

- Deep brain stimulation (DBS)
- Functional stimulation (FES)
- Cardiac defibrillation (CDF)

---

---

---

---


---

---

---

---

**Bioelectricity: key concepts**



**Electricity**

*The set of physical phenomena associated with the presence and flow of electric charge*

---

---

---

---

---

---

---

---

## Bioelectricity: key concepts



### Electricity

*The set of physical phenomena associated with the presence and flow of electric charge*

- Charge  $\stackrel{\text{def}}{=}$  *A property of subatomic particles determining their electromagnetic interactions*

---

---

---

---

---

---

---

---

## Bioelectricity: key concepts




### Electricity

*The set of physical phenomena associated with the presence and flow of electric charge*

- Charge  $\stackrel{\text{def}}{=}$  *A property of subatomic particles determining their electromagnetic interactions*

Atoms have particles with positive (**protons**) and negative (**electrons**) charge

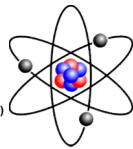● electron (-)  
● proton (+)  
● neutron



---

---

---

---

---

---

---

---

## Bioelectricity: key concepts



### Electricity

*The set of physical phenomena associated with the presence and flow of electric charge*

- Charge  $\stackrel{\text{def}}{=}$  *A property of subatomic particles determining their electromagnetic interactions*
- Electric current  $\stackrel{\text{def}}{=}$  *A movement or flow of electrically charged particles through a medium*

---

---

---

---

---

---

---

---


## Bioelectricity: key concepts


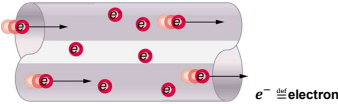
### Electricity

The set of physical phenomena associated with the presence and flow of electric charge

- Charge  $\stackrel{\text{def}}{=} A$  property of subatomic particles determining their electromagnetic interactions
- Electric current  $\stackrel{\text{def}}{=} A$  movement or flow of electrically charged particles through a medium



---

---

---

---

---

---

---

---


## Bioelectricity: key concepts


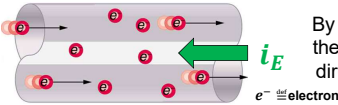
### Electricity

The set of physical phenomena associated with the presence and flow of electric charge

- Charge  $\stackrel{\text{def}}{=} A$  property of subatomic particles determining their electromagnetic interactions
- Electric current  $\stackrel{\text{def}}{=} A$  movement or flow of electrically charged particles through a medium



By definition, the direction of the current  $i_E$  is given by the direction of positive charges

---

---

---

---

---

---

---

---

## Bioelectricity: key concepts



### Electricity

The set of physical phenomena associated with the presence and flow of electric charge

- Charge  $\stackrel{\text{def}}{=} A$  property of subatomic particles determining their electromagnetic interactions
- Electric current  $\stackrel{\text{def}}{=} A$  movement or flow of electrically charged particles through a medium
- Voltage  $\stackrel{\text{def}}{=} The$  work required to move a unit charge between two points

---

---

---

---

---

---


---

---

## Electric charge



- electron (-)
- proton (+)
- neutron

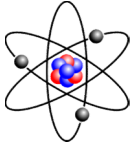

---

---

---

---

---

---

---


---

## Electric charge



It is **quantized**, i.e., it comes in integer multiples of an individual small unit called "**elementary charge**"  $e$

- electron (-)
- proton (+)
- neutron

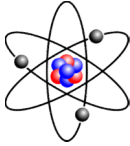

---

---

---

---

---

---

---

---


## Electric charge



It is **quantized**, i.e., it comes in integer multiples of an individual small unit called "**elementary charge**"  $e$

In the SI, it is measured in **Coulomb (C)**

- electron (-)
- proton (+)
- neutron

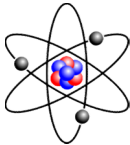

---

---

---

---

---

---

---


---

## Electric charge



It is **quantized**, i.e., it comes in integer multiples of an individual small unit called "**elementary charge**"  $e$

- electron (-)
- proton (+)
- neutron

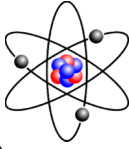

In the SI, it is measured in **Coulomb (C)**

$$e \cong 1.602 \times 10^{-19} \text{ C}$$

$$1 \text{ C} = e / (1.602 \times 10^{-19}) \cong 6.241 \times 10^{18} e$$

---

---

---

---

---

---

---


---

## Electric charge



It is **quantized**, i.e., it comes in integer multiples of an individual small unit called "**elementary charge**"  $e$

- electron (-)
- proton (+)
- neutron

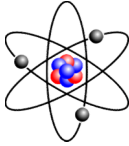

In the SI, it is measured in **Coulomb (C)**

$$e \cong 1.602 \times 10^{-19} \text{ C}$$

$$1 \text{ C} = e / (1.602 \times 10^{-19}) \cong 6.241 \times 10^{18} e$$

An electron and a proton have both the charge of  $1 e$  but opposite sign ( $e^-$  and  $e^+$ , respectively)

---

---

---

---


---

---

---

---

## Electric current

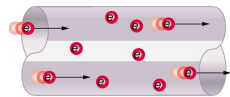

---

---

---

---

---

---


---

---
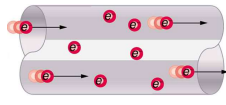
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



---

---

---

---

---

---


---

---
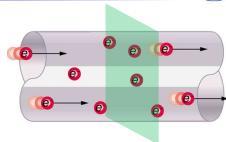
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



A flow of positive charges gives the same electric current and has the same effect in the circuit as an equal flow of negative charges in the opposite direction

---

---

---

---

---

---


---

---
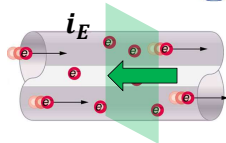
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



A flow of positive charges gives the same electric current and has the same effect in the circuit as an equal flow of negative charges in the opposite direction

A convention is that a **positive current** flows in the same direction as **positive charges** and vice versa

---

---

---

---

---

---

---


---


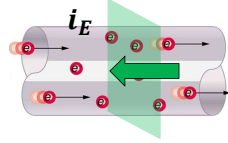
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



In the SI, it is measured in **Ampere (A)**

$$1 \text{ A} = 1 \text{ C} / 1 \text{ s}$$

---

---

---

---

---

---


---

---
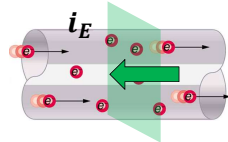
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



In the SI, it is measured in **Ampere (A)**

$$1 \text{ A} = 1 \text{ C} / 1 \text{ s}$$

If we denote with  $\Delta Q(t)$  the amount of charge that flows in the interval  $[t, t + \Delta t]$ , then

$$i_E(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q(t)}{\Delta t} = \dot{Q}(t)$$

---

---

---

---

---

---


---

---
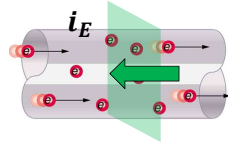
## Electric current



It is caused by moving electrons (e.g., in a circuit), ions (e.g., in a battery), or both (e.g., in plasma)



In the SI, it is measured in **Ampere (A)**

$$1 \text{ A} = 1 \text{ C} / 1 \text{ s}$$

If we denote with  $\Delta Q(t)$  the amount of charge that flows in the interval  $[t, t + \Delta t]$ , then

$$i_E(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q(t)}{\Delta t} = \dot{Q}(t) \text{ It's a derivative!}$$

---

---

---

---

---

---


---

---
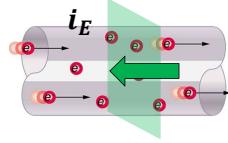
## Electric current



We usually consider two classes of electric currents:



---

---

---

---

---

---

---


---
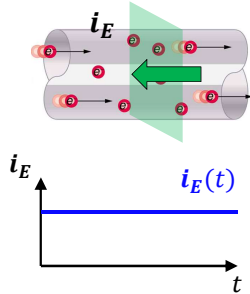
## Electric current



We usually consider two classes of electric currents:

□ **Direct (DC)**, i.e., the flow of charge is **unidirectional**



---

---

---

---

---

---

---


---
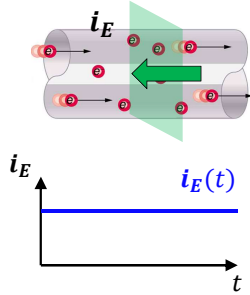
## Electric current



We usually consider two classes of electric currents:

□ **Direct (DC)**, i.e., the flow of charge is **unidirectional**



*It is produced by sources like batteries, thermocouples, solar cells, and commutator-type electric machines of the dynamo type*

---

---

---

---

---

---

---


---
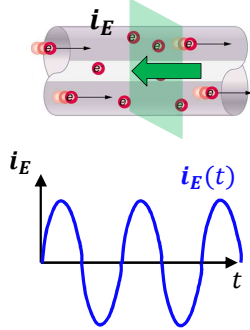
## Electric current



We usually consider two classes of electric currents:

- **Direct (DC)**, i.e., the flow of charge is **unidirectional**
- **Alternating (AC)**, i.e., the movement of the charges **periodically reverses** direction



---

---

---

---

---

---


---

---
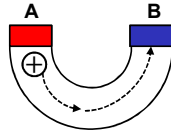
## Voltage



It is the work associated with moving a unit charge between two points along a circuit



---

---

---

---

---

---


---

---
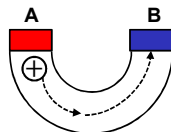
## Voltage



It is the work associated with moving a unit charge between two points along a circuit



In the SI, it is measured in **Volts (V)**

$$1 \text{ V} = 1 \text{ J} / 1 \text{ C} \quad \text{J} = \text{joule}$$

---

---

---

---

---

---


---

---
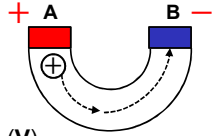
## Voltage



It is the work associated with moving a unit charge between two points along a circuit



In the SI, it is measured in **Volts (V)**

$$1 \text{ V} = 1 \text{ J} / 1 \text{ C} \quad \text{J} = \text{joule}$$

By definition, **positive charges** are pulled towards **lower voltages**. The opposite is for negative charges

---

---

---

---

---

---


---

---
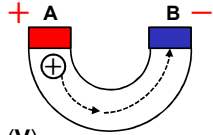
## Voltage



It is the work associated with moving a unit charge between two points along a circuit



In the SI, it is measured in **Volts (V)**

$$1 \text{ V} = 1 \text{ J} / 1 \text{ C} \quad \text{J} = \text{joule}$$

By definition, **positive charges** are pulled towards **lower voltages**. The opposite is for negative charges

Current flows from lower voltage to higher voltage only when a source of energy "pushes" it (**battery**)

---

---

---

---

---

---

---

---

## Electric power



It is the **rate** at which work is done along a circuit

---

---

---

---

---

---

---

---

## Electric power


It is the **rate** at which work is done along a circuit

$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$

$$P = \frac{\Delta W}{\Delta t}$$

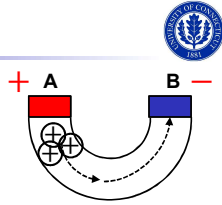

---

---

---

---

---

---

---

---

## Electric power


It is the **rate** at which work is done along a circuit

$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$
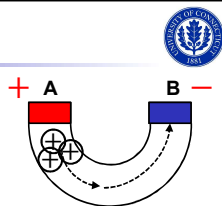
$$P = \frac{\Delta W \cdot \Delta q}{\Delta q \cdot \Delta t}$$



---

---

---

---

---

---

---

---

## Electric power

It is the **rate** at which work is done along a circuit


$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$

$$P = \frac{\Delta W}{\Delta q \cdot \Delta t} \cdot \Delta q$$

voltage

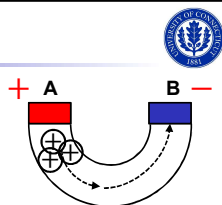

---

---

---

---

---

---

---

---

## Electric power



It is the **rate** at which work is done along a circuit


$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$

$$P = \frac{\Delta W}{\Delta t} = \frac{\Delta W}{\Delta q} \cdot \frac{\Delta q}{\Delta t}$$

*current*

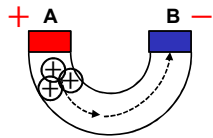

---

---

---

---

---

---

---

---

## Electric power




It is the **rate** at which work is done along a circuit

$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$

$$P = v \cdot i$$

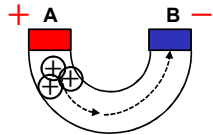

---

---

---

---

---

---

---

---

## Electric power



It is the **rate** at which work is done along a circuit


$\Delta q$  <sup>def</sup> amount of charge moved from A to B

$\Delta W$  <sup>def</sup> work done moving  $\Delta q$  from A to B

$\Delta t$  <sup>def</sup> time to do work  $\Delta W$

In the SI, it is measured in **Watts (W)**
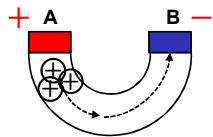
$$1 \text{ W} = 1 \text{ J} / 1 \text{ s} = 1 \text{ V} \times 1 \text{ A}$$



---

---

---

---


---

---

---

---

### Polarity of power

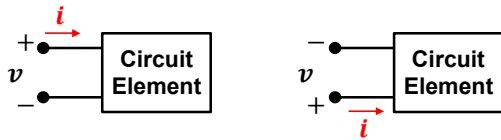

---

---

---

---


---

---

---

---

### Polarity of power

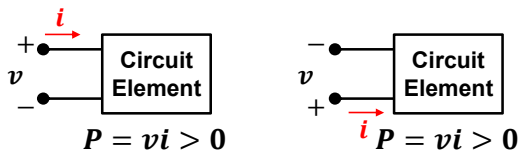

A positive value for power indicates that power is being absorbed (or consumed) by the circuit element

---

---

---

---


---

---

---

---

### Polarity of power

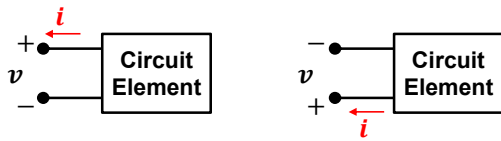

---

---

---

---


---

---


---

---

## Polarity of power

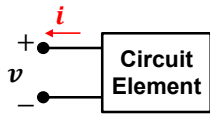

$$P = -vi < 0$$

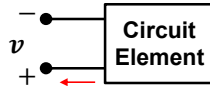

$$P = -vi < 0$$

A negative value for power says that power is being generated by (or extracted from) the circuit element (e.g., **battery**)

---

---

---

---

---

---

---

---

## A circuit element is...



### □ Active

$P < 0$ , i.e., it can generate energy



voltage generator



batteries

---

---

---

---

---

---

---

---

## A circuit element is...



### □ Active

$P < 0$ , i.e., it can generate energy



voltage generator



batteries

### □ Passive

$P \geq 0$ , i.e., it dissipates or stores energy



resistor



capacitor



inductor

---

---

---

---

---

---

---


---


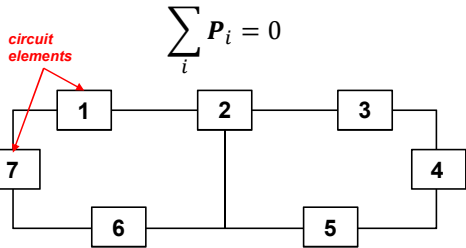
## Remember...



In any **closed electric circuit** the amount of power that is supplied must be equal to the amount that is absorbed



---

---

---

---

---

---


---

---
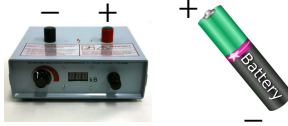
## Source



- It is an **active** circuit element with **two terminals** that provides energy to the circuit



---

---

---

---

---

---


---

---
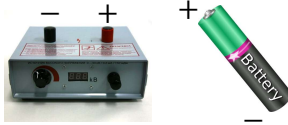
## Source



- It is an **active** circuit element with **two terminals** that provides energy to the circuit



- There is no direct voltage-current ( $v-i$ ) relationship for a source.  $v$  and  $i$  depend on the type of circuit

---

---

---

---

---

---


---

---
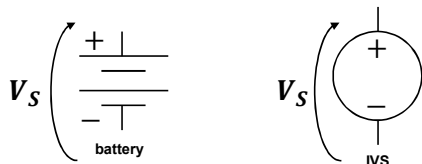
## Ideal sources



An **ideal voltage source (IVS)** generates a prescribed voltage at its terminals **regardless of the current flow**



---

---

---

---

---

---


---

---
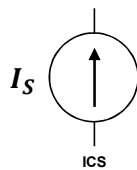
## Ideal sources



An **ideal current source (ICS)** provides a prescribed amount of current **regardless of the voltage** at its terminals



---

---

---

---

---

---


---

---
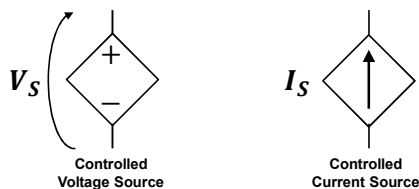
## Controlled sources



A voltage or current source is **controlled** if its output (voltage or current) depends on the voltage or current somewhere else in the circuit



---

---

---

---


---

---

---

---

## Examples

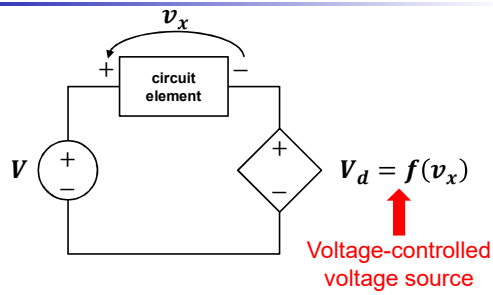

---

---

---

---


---

---

---

---

## Examples

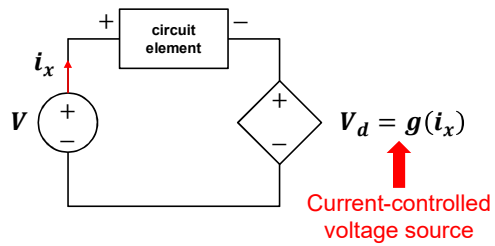

---

---

---

---

---

---

---

---

## Resistor



A circuit element that limits the flow of current through it, i.e., it opposes the current by producing a voltage drop between the terminals



---

---

---

---

---

---


---

---
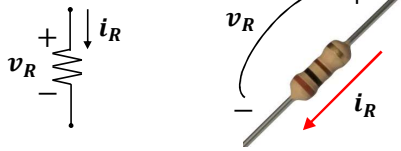
## Resistor



A circuit element that limits the flow of current through it, i.e., it opposes the current by producing a voltage drop between the terminals



---

---

---

---

---

---


---

---
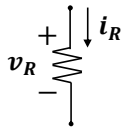
## Resistor



A circuit element that limits the flow of current through it, i.e., it opposes the current by producing a voltage drop between the terminals



The ability to impede current is called **resistance (R)** and is measured in **ohms ( $\Omega$ )**

$$1 \Omega = 1 \text{ V} / 1 \text{ A}$$

---

---

---

---

---

---


---

---
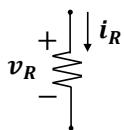
## Resistor



A circuit element that limits the flow of current through it, i.e., it opposes the current by producing a voltage drop between the terminals



The inverse of the resistance is the **conductance (G)** and is measured in **siemens (S)**

$$1 \text{ S} = 1 \text{ A} / 1 \text{ V}$$

---

---

---

---

---

---


---

---
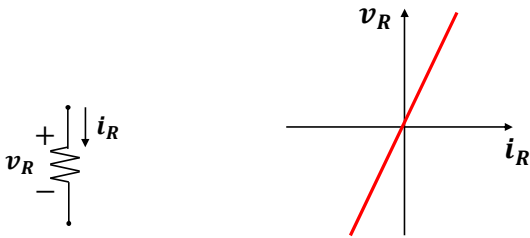
### Ohm's law



- An ideal resistor is characterized by a **linear** voltage-current relationship



---

---

---

---

---

---


---

---
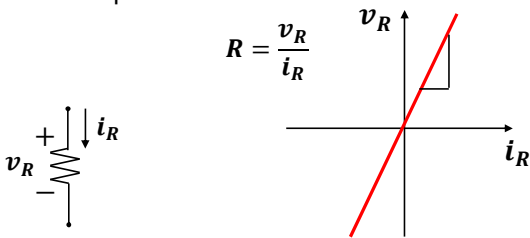
### Ohm's law



- An ideal resistor is characterized by a **linear** voltage-current relationship
- The slope is the resistance:



---

---

---

---

---

---


---

---
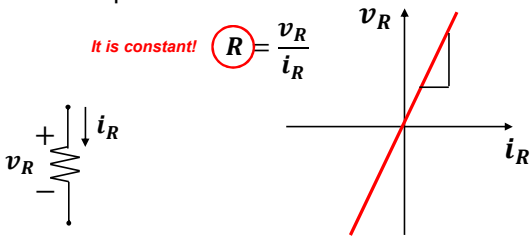
### Ohm's law



- An ideal resistor is characterized by a **linear** voltage-current relationship
- The slope is the resistance:



---

---

---

---

---

---


---

---
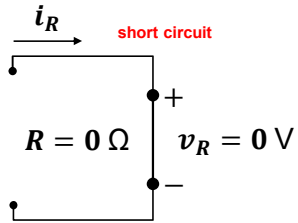
### Ohm's law ( $v_R = R \cdot i_R$ )



- An ideal bare wire connecting circuit elements together has resistance  $R = 0 \Omega$




---

---

---

---

---

---


---

---
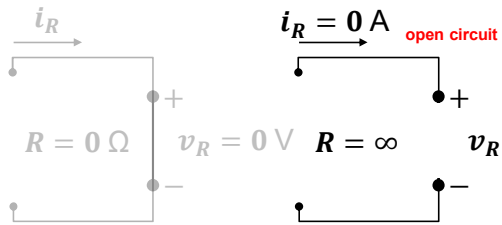
### Ohm's law ( $i_R = v_R/R$ )



- An ideal bare wire connecting circuit elements together has resistance  $R = 0 \Omega$
- A gap between circuit elements has  $R = \infty$




---

---

---

---


---

---

---

---

### An example

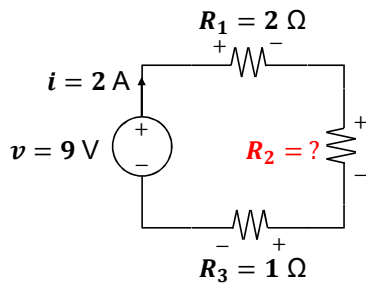


---

---

---

---


---

---

---

---

An example

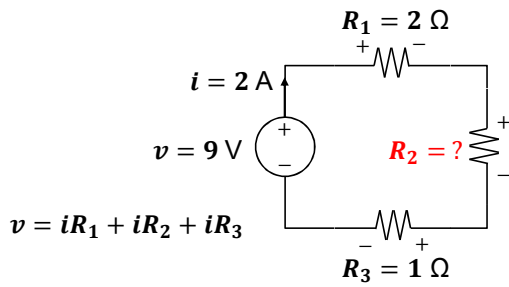


---

---

---

---


---

---

---

---

An example

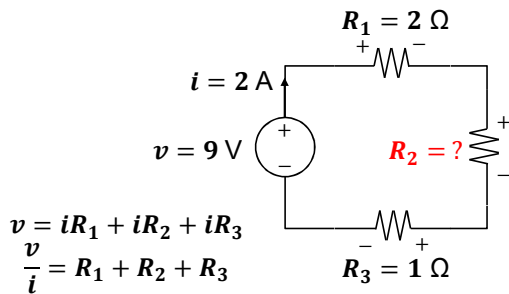


---

---

---

---


---

---

---

---

An example

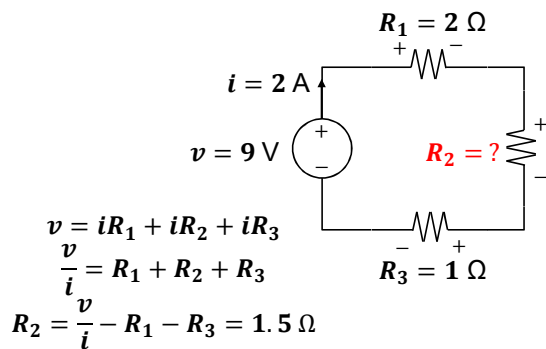


---

---

---

---

---

---

---

---

### Power and Ohm's law



For an ideal resistor the power is:

$$P = v_R \cdot i_R = (i_R R) \cdot i_R = i_R^2 R$$

---

---

---

---

---

---

---

---

### Power and Ohm's law



For an ideal resistor the power is:

$$P = v_R \cdot i_R = (i_R R) \cdot i_R = i_R^2 R$$

- $P > 0$  independently of the signs of  $i_R$  and  $v_R$  (i.e., power is always absorbed)

---

---

---

---

---

---

---

---

### Power and Ohm's law



For an ideal resistor the power is:

$$P = v_R \cdot i_R = (i_R R) \cdot i_R = i_R^2 R$$

- $P > 0$  independently of the signs of  $i_R$  and  $v_R$  (i.e., power is always absorbed)
- The resistor dissipates the absorbed power as heat

---

---

---

---

---

---

---

---



## Exceptions to Ohm's law



- ❑ Ohm's law does not apply at very high voltages and currents (nonlinear  $i$ - $v$  relationships occur)
- ❑ Many physiological systems only follow Ohm's law in a narrow range of voltages. Outside this range the model is nonlinear
- ❑ Different materials exhibit different resistances. Some materials exhibit linear behavior over a limited range of voltage and current values

---

---

---

---

---

---

---

---