

## Circuit Analysis Part II

ENGR 1166 Biomedical Engineering

---

---

---

---

---

---

---

---

### Recap



- ❑ **KCL:** At any node in an electrical circuit, the algebraic sum of the currents is equal to zero
- ❑ **KVL:** the directed sum of voltages along any closed path in an electrical circuit is zero
- ❑ **Ohm's law:** the ratio between the voltage drop at the terminals of an ideal resistor and the current passing through it is constant and is called "resistance"

---

---

---

---

---

---

---

---

### Recap



- ❑ **Equivalent resistance:** Any circuit of resistors can be replaced with a single equivalent resistance
- ❑ **VDR:** A rule to compute the voltage drop across each resistor in a series of resistors
- ❑ **CDR:** A rule to compute the current through each resistor in a parallel circuit

*These tools are introduced for circuits made of resistors only!*

---

---

---

---


---

---

---

---

### Analysis of a more general circuit

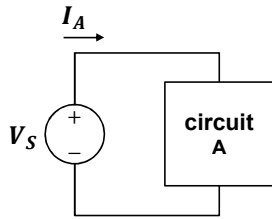

How to solve a circuit problem (e.g., compute unknown voltages and currents) when the circuit includes elements other than resistors?

---

---

---

---


---

---

---

---

### Analysis of a more general circuit

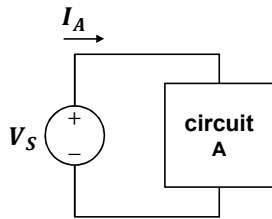

The **node-voltage method** is a technique to **systematically** solve a circuit problem when elements other than resistors are involved

---

---

---

---


---

---

---

---

### Our goal

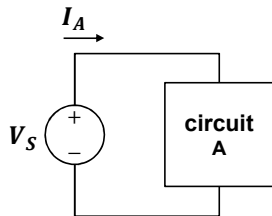

If there are  $N$  nodes in the circuit, we want to determine up to  $N - 1$  equations with  $N - 1$  unknown variables and then solve

---

---

---

---

---

---


---

---

### Node-voltage method



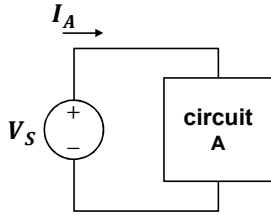- 1) Set one **essential** node of circuit A as a reference (**ground**) and refer the voltage across any element in circuit A to it



---

---

---

---

---

---


---

---

### Node-voltage method



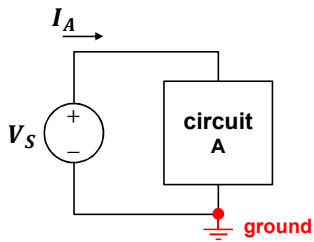- 1) Set one **essential** node of circuit A as a reference (**ground**) and refer the voltage across any element in circuit A to it



---

---

---

---

---

---


---

---

### Node-voltage method



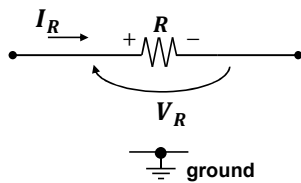- 1) Set one **essential** node of circuit A as a reference (**ground**) and refer the voltage across any element in circuit A to it



---

---

---

---

---

---


---

---

## Node-voltage method



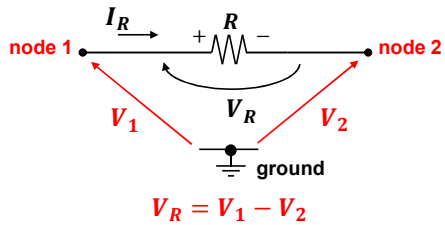- 1) Set one **essential** node of circuit A as a reference (**ground**) and refer the voltage across any element in circuit A to it



---

---

---

---

---

---

---

---

## Node-voltage method



- 2) Except for the ground, write the KCL at every **essential** node in circuit A

---

---

---

---

---

---


---

---

## Node-voltage method



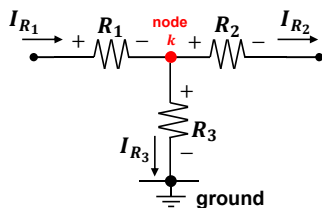- 2) Except for the ground, write the KCL at every **essential** node in circuit A



---

---

---

---

---

---


---

---

## Node-voltage method



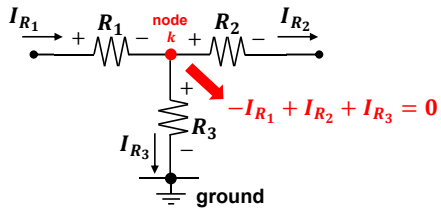- 2) Except for the ground, write the KCL at every **essential** node in circuit A



---

---

---

---

---

---

---

---

## Node-voltage method



- 3) Use the Ohm's law to write the currents as a function of the voltages at the terminals

---

---

---

---

---

---


---

---

## Node-voltage method



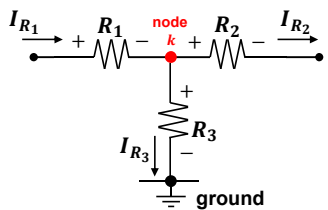- 3) Use the Ohm's law to write the currents as a function of the voltages at the terminals



---

---

---

---

---

---


---

---

### Node-voltage method



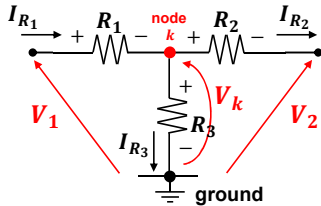3) Use the Ohm's law to write the currents as a function of the voltages at the terminals



---

---

---

---

---

---


---

---

### Node-voltage method



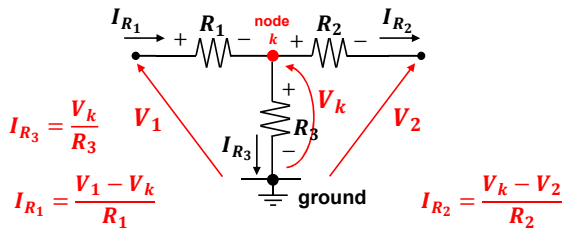3) Use the Ohm's law to write the currents as a function of the voltages at the terminals



---

---

---

---

---

---

---

---

### Node-voltage method



4) Replace the voltages in the KCL equations

---

---

---

---

---

---

---

---

### Node-voltage method



4) Replace the voltages in the KCL equations

$$-I_{R_1} + I_{R_2} + I_{R_3} = 0$$

---

---

---

---

---

---

---

---

### Node-voltage method



4) Replace the voltages in the KCL equations

$$-I_{R_1} + I_{R_2} + I_{R_3} = 0$$



$$-\frac{V_1 - V_k}{R_1} + \frac{V_k - V_2}{R_2} + \frac{V_k}{R_3} = 0$$

---

---

---

---

---

---

---

---

### Node-voltage method



4) Replace the voltages in the KCL equations

$$-I_{R_1} + I_{R_2} + I_{R_3} = 0$$



$$-\frac{V_1 - V_k}{R_1} + \frac{V_k - V_2}{R_2} + \frac{V_k}{R_3} = 0$$



$$V_k = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \cdot \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

---

---

---

---

---

---

---

---

## Node-voltage method



**NOTE:** I use KCL at the nodes to set the equations and I use Ohm's law to introduce voltages in these equations



*I will solve with respect to voltages!*

---

---

---

---

---

---


---

---
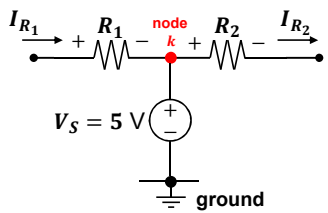
## Node-voltage method



**NOTE:** If there is a voltage source between a node and the ground, there is no need to use KCL at that node as the voltage is known



---

---

---

---

---

---


---

---
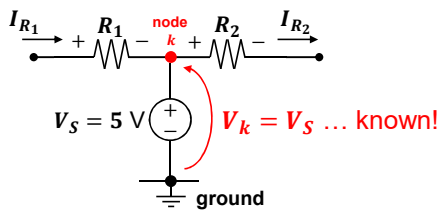
## Node-voltage method



**NOTE:** If there is a voltage source between a node and the ground, there is no need to use KCL at that node as the voltage is known



---

---

---

---

---


---

---

---



### Example 1

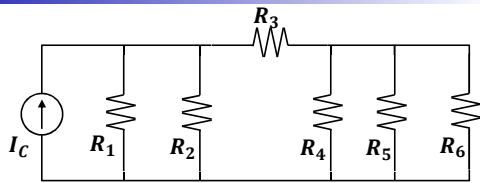

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

What is the voltage at each circuit element?

---

---

---

---


---

---

---

---

### Example 1: where are the nodes?

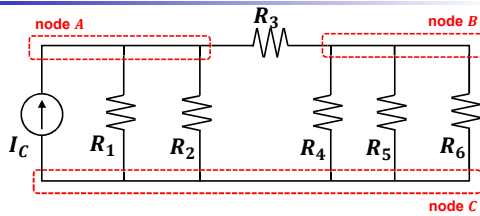

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

---

---

---

---


---

---

---

---

### Example 1: set the ground

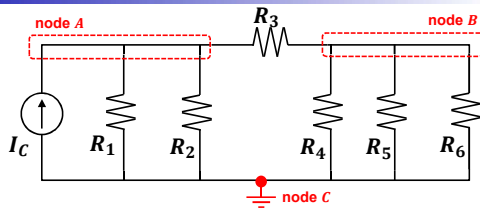

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

---

---

---

---


---

---

---

---

### Example 1: set the current flow

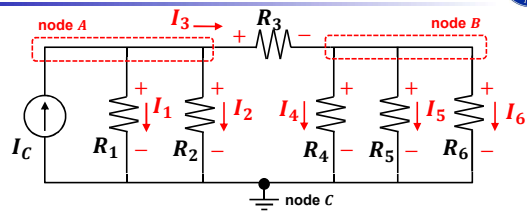

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

**NOTE:** if not specified by the problem, we guess the direction of the currents now and we will fix it later when we have the solution

---

---

---

---


---

---

---

---

### Example 1: KCL

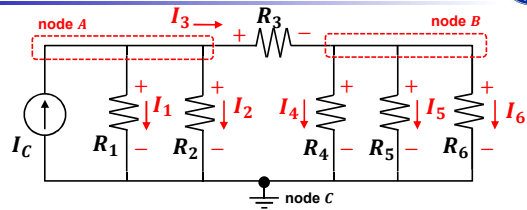

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

$$\text{node A: } -I_C + I_1 + I_2 + I_3 = 0$$

$$\text{node B: } -I_3 + I_4 + I_5 + I_6 = 0$$

---

---

---

---


---

---

---

---

### Example 1: voltages

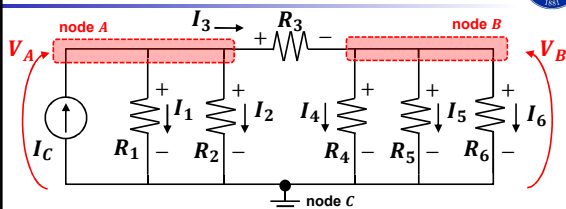

$R_1 = 1 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 1 \Omega$ ;  $R_4 = 12 \Omega$ ;  $R_5 = 12 \Omega$ ;  
 $R_6 = 12 \Omega$ ;  $I_C = 5A$

$$I_1 = V_A/R_1; I_2 = V_A/R_2; I_3 = (V_A - V_B)/R_3$$

$$I_4 = V_B/R_4; I_5 = V_B/R_5; I_6 = V_B/R_6$$

---

---

---

---

---

---

---

---

### Example 1: voltages



$$\begin{aligned} \text{node A: } & -I_C + I_1 + I_2 + I_3 = 0 \\ \text{node B: } & -I_3 + I_4 + I_5 + I_6 = 0 \end{aligned}$$



$$\begin{aligned} \text{node A: } & -I_C + \frac{V_A}{R_1} + \frac{V_A}{R_2} + \frac{V_A - V_B}{R_3} = 0 \\ \text{node B: } & -\frac{V_A - V_B}{R_3} + \frac{V_B}{R_4} + \frac{V_B}{R_5} + \frac{V_B}{R_6} = 0 \end{aligned}$$

$$R_1 = 1 \Omega; R_2 = 2 \Omega; R_3 = 1 \Omega; R_4 = 12 \Omega; R_5 = 12 \Omega; \\ R_6 = 12 \Omega; I_C = 5A$$

---

---

---

---

---

---

---

---

### Example 1: solve!



$$\begin{aligned} \text{node A: } & -I_C + I_1 + I_2 + I_3 = 0 \\ \text{node B: } & -I_3 + I_4 + I_5 + I_6 = 0 \end{aligned}$$



$$\begin{aligned} \text{node A: } & \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_A - \frac{1}{R_3} V_B = I_C \\ \text{node B: } & \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} \right) V_B - \frac{1}{R_3} V_A = 0 \end{aligned}$$

$$R_1 = 1 \Omega; R_2 = 2 \Omega; R_3 = 1 \Omega; R_4 = 12 \Omega; R_5 = 12 \Omega; \\ R_6 = 12 \Omega; I_C = 5A$$

---

---

---

---

---

---

---

---

### Example 1: solve!



$$\begin{aligned} \text{node A: } & -I_C + I_1 + I_2 + I_3 = 0 \\ \text{node B: } & -I_3 + I_4 + I_5 + I_6 = 0 \end{aligned}$$



$$\begin{aligned} \frac{5}{2} V_A - V_B &= 5 \\ \frac{5}{4} V_B - V_A &= 0 \end{aligned}$$

$$R_1 = 1 \Omega; R_2 = 2 \Omega; R_3 = 1 \Omega; R_4 = 12 \Omega; R_5 = 12 \Omega; \\ R_6 = 12 \Omega; I_C = 5A$$

---

---

---

---

---

---

---

---

### Example 1: solve!



$$\begin{aligned} \text{node A: } -I_C + I_1 + I_2 + I_3 &= 0 \\ \text{node B: } -I_3 + I_4 + I_5 + I_6 &= 0 \end{aligned}$$



$$\begin{aligned} V_B &\cong 2.35 \text{ V} \\ V_A &\cong 2.94 \text{ V} \end{aligned}$$

---

---

---

---


---

---

---

---

### Example 2

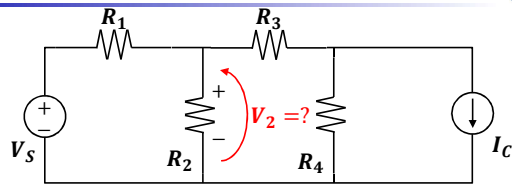

$$\begin{aligned} R_1 &= 1/2 \ \Omega; R_2 = 1/3 \ \Omega; R_3 = 1/2 \ \Omega; R_4 = 1/4 \ \Omega; \\ V_S &= 5 \text{ V}; I_C = 3 \text{ A} \end{aligned}$$

---

---

---

---


---

---

---

---

### Example 2: where are the nodes?

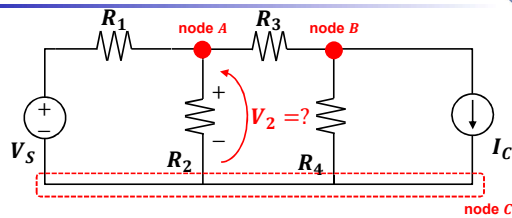

$$\begin{aligned} R_1 &= 1/2 \ \Omega; R_2 = 1/3 \ \Omega; R_3 = 1/2 \ \Omega; R_4 = 1/4 \ \Omega; \\ V_S &= 5 \text{ V}; I_C = 3 \text{ A} \end{aligned}$$

---

---

---

---


---

---

---

---

### Example 2: set the ground

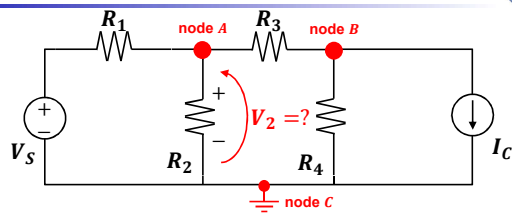

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

---

---

---

---


---

---

---

---

### Example 2: set the current flow

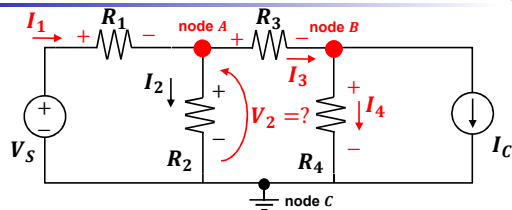

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

**NOTE:** The direction of  $I_2$  and  $I_C$  is set by the problem while we need to guess the direction of the remaining currents

---

---

---

---


---

---

---

---

### Example 2: KCL

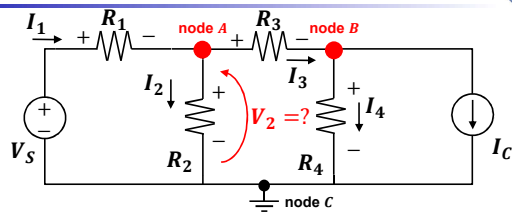

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

node A:  $-I_1 + I_2 + I_3 = 0$   
 node B:  $-I_3 + I_4 + I_C = 0$

---

---

---

---


---

---

---

---

### Example 2: voltages

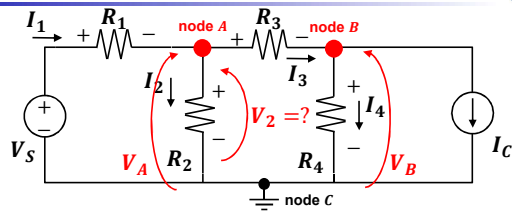

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

$$I_1 = (V_S - V_A)/R_1; \quad I_2 = V_A/R_2; \quad V_2 = V_A$$

$$I_3 = (V_A - V_B)/R_3; \quad I_4 = V_B/R_4$$

---

---

---

---

---

---

---

---

### Example 2: voltages



$$\text{node A: } -I_1 + I_2 + I_3 = 0$$

$$\text{node B: } -I_3 + I_4 + I_C = 0$$



$$\text{node A: } -\frac{V_S - V_A}{R_1} + \frac{V_A}{R_2} + \frac{V_A - V_B}{R_3} = 0$$

$$\text{node B: } -\frac{V_A - V_B}{R_3} + \frac{V_B}{R_4} + I_C = 0$$

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

---

---

---

---

---

---

---

---

### Example 2: solve!



$$\text{node A: } -I_1 + I_2 + I_3 = 0$$

$$\text{node B: } -I_3 + I_4 + I_C = 0$$



$$\text{node A: } \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)V_A - \frac{1}{R_3}V_B - \frac{1}{R_1}V_S = 0$$

$$\text{node B: } \left(\frac{1}{R_3} + \frac{1}{R_4}\right)V_B - \frac{1}{R_3}V_A + I_C = 0$$

$R_1 = 1/2 \Omega$ ;  $R_2 = 1/3 \Omega$ ;  $R_3 = 1/2 \Omega$ ;  $R_4 = 1/4 \Omega$ ;  
 $V_S = 5 \text{ V}$ ;  $I_C = 3 \text{ A}$

---

---

---

---

---

---

---

---

### Example 2: solve!



$$\begin{aligned} \text{node A: } -I_1 + I_2 + I_3 &= 0 \\ \text{node B: } -I_3 + I_4 + I_C &= 0 \end{aligned}$$



$$\begin{aligned} 7V_A - 2V_B - 10 &= 0 \\ 6V_B - 2V_A + 3 &= 0 \end{aligned}$$

---

---

---

---

---

---

---

---

### Example 2: solve!



$$\begin{aligned} \text{node A: } -I_1 + I_2 + I_3 &= 0 \\ \text{node B: } -I_3 + I_4 + I_C &= 0 \end{aligned}$$



$$\begin{aligned} V_A &= 3V_B + 3/2 \\ 21V_B + 21/2 - 2V_B - 10 &= 0 \end{aligned}$$



$$\begin{aligned} V_A &= \frac{27}{19} \cong 1.42 \text{ V} \\ V_B &= -\frac{1}{38} \cong -0.03 \text{ V} \end{aligned}$$

---

---

---

---


---

---

---

---

### Example 3

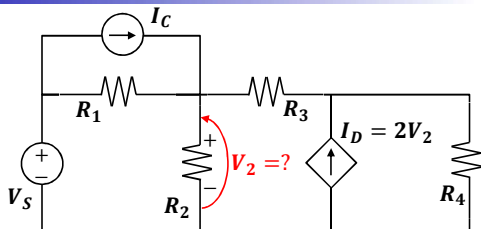

$$R_1 = 2 \Omega; R_2 = 3 \Omega; R_3 = 4 \Omega; R_4 = 5 \Omega; V_S = 3 \text{ V}; I_C = 2 \text{ A}$$

---

---

---

---


---

---

---

---

### Example 3: where are the nodes?

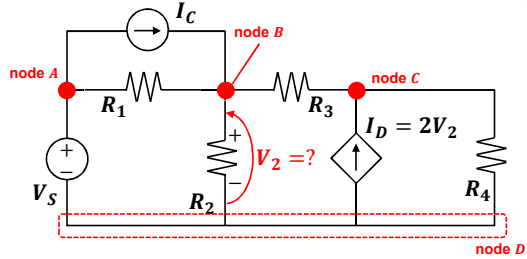

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

---

---

---

---


---

---

---

---

### Example 3: set the ground

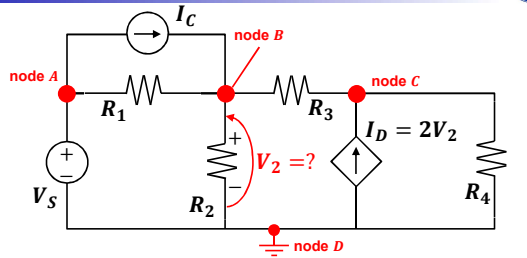

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

---

---

---

---


---

---

---

---

### Example 3: set the current flow

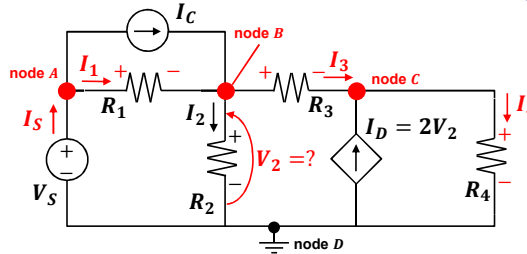

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

**NOTE:** The direction of  $I_2$ ,  $I_C$ , and  $I_D$  is set by the problem

---

---

---

---

---


---

---

---



### Example 3: KCL

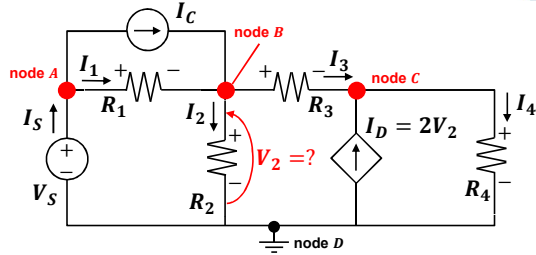

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

$$\text{node A: } -I_S + I_C + I_1 = 0$$

$$\text{node B: } -I_1 - I_C + I_2 + I_3 = 0$$

$$\text{node C: } -I_3 - I_D + I_4 = 0$$

---

---

---

---

---

---


---

---

---

---

### Example 3: voltages

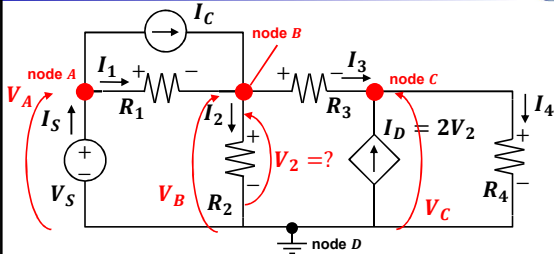

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

---

---

---

---

---

---


---

---

---

---

### Example 3: voltages

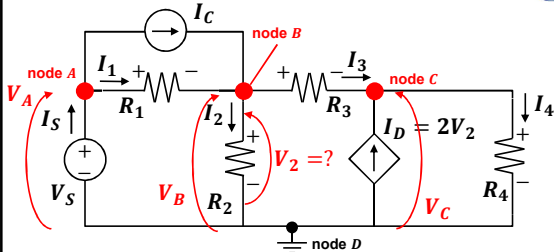

$R_1 = 2 \Omega$ ;  $R_2 = 3 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 5 \Omega$ ;  $V_S = 3 \text{ V}$ ;  $I_C = 2 \text{ A}$

**NOTE:**  $V_A = V_S = 3 \text{ V}$ ... we do not need KCL at node A!

---

---

---

---

---

---


---

---

---

---

### Example 3: voltages

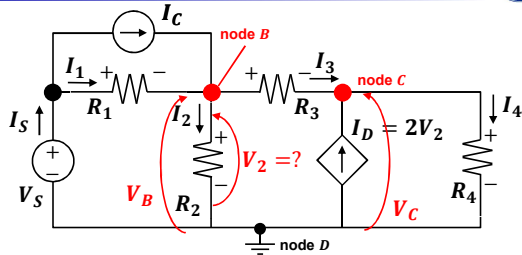

$R_1 = 2 \Omega; R_2 = 3 \Omega; R_3 = 4 \Omega; R_4 = 5 \Omega; V_S = 3 \text{ V}; I_C = 2 \text{ A}$

$$I_1 = (V_S - V_B)/R_1; I_2 = V_B/R_2; V_2 = V_B$$

$$I_3 = (V_B - V_C)/R_3; I_4 = V_C/R_4$$

---

---

---

---

---

---

---

---

---

---

### Example 3: voltages



$$\text{node B: } -I_1 - I_C + I_2 + I_3 = 0$$

$$\text{node C: } -I_3 - I_D + I_4 = 0$$



$$\text{node B: } -\frac{V_S - V_B}{R_1} - I_C + \frac{V_B}{R_2} + \frac{V_B - V_C}{R_3} = 0$$

$$\text{node C: } -\frac{V_B - V_C}{R_3} - 2V_B + \frac{V_C}{R_4} = 0$$

$R_1 = 2 \Omega; R_2 = 3 \Omega; R_3 = 4 \Omega; R_4 = 5 \Omega; V_S = 3 \text{ V}; I_C = 2 \text{ A}$

---

---

---

---

---

---

---

---

---

---

### Example 3: solve!



$$\text{node B: } -I_1 - I_C + I_2 + I_3 = 0$$

$$\text{node C: } -I_3 - I_D + I_4 = 0$$



$$\text{node B: } \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)V_B - \frac{1}{R_3}V_C - \frac{1}{R_1}V_S - I_C = 0$$

$$\text{node C: } \left(\frac{1}{R_3} + \frac{1}{R_4}\right)V_C - \left(2 + \frac{1}{R_3}\right)V_B = 0$$

$R_1 = 2 \Omega; R_2 = 3 \Omega; R_3 = 4 \Omega; R_4 = 5 \Omega; V_S = 3 \text{ V}; I_C = 2 \text{ A}$

---

---

---

---

---

---

---

---

---

---

Example 3: solve!



$$\begin{aligned}\text{node B: } & -I_1 - I_C + I_2 + I_3 = 0 \\ \text{node C: } & -I_3 - I_D + I_4 = 0\end{aligned}$$



$$\begin{aligned}\frac{13}{12}V_B - \frac{1}{4}V_C - \frac{3}{2} - 2 &= 0 \\ \frac{9}{20}V_C - \frac{9}{4}V_B &= 0\end{aligned}$$

---

---

---

---

---

---

---

---

Example 3: solve!



$$\begin{aligned}\text{node B: } & -I_1 - I_C + I_2 + I_3 = 0 \\ \text{node C: } & -I_3 - I_D + I_4 = 0\end{aligned}$$



$$\begin{aligned}V_C &= 5V_B \\ \frac{13}{12}V_B - \frac{5}{4}V_B &= \frac{7}{2}\end{aligned}$$



$$\begin{aligned}V_B &= -21 \text{ V} \\ V_C &= -105 \text{ V}\end{aligned}$$

---

---

---

---

---

---

---

---