

Circuit Analysis Part I


ENGR 1166 Biomedical Engineering

Recap



- **KCL:** At any node in an electrical circuit, the algebraic sum of the currents is equal to zero
- **KVL:** the directed sum of voltages along any closed path in an electrical circuit is zero
- **Ohm's law:** the ratio between the voltage drop at the terminals of an ideal resistor and the current passing through it is constant and is called "resistance"

Circuit equivalency

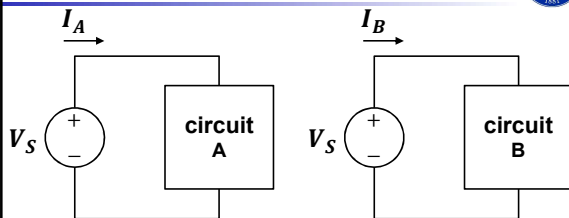

Two circuits are **equivalent** if they cannot be distinguished from each other by voltage and current measurements, i.e., if they **behave identically**

Circuit equivalency

In this case, since V_S is applied to both circuits:
 Circuit A and B are equivalent $\Leftrightarrow I_A = I_B$


Circuit equivalency

Sometimes it is useful to replace a complex circuit with an equivalent one that is much simpler to study

Circuit equivalency


Here we will assume that the circuits to be replaced ("reduced") are **made of resistors only** (i.e., passive circuits)

An example of circuit equivalency

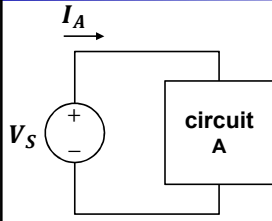

- Circuit A is any combination of resistors
- The voltage at the terminals of circuit A is V_S

An example of circuit equivalency

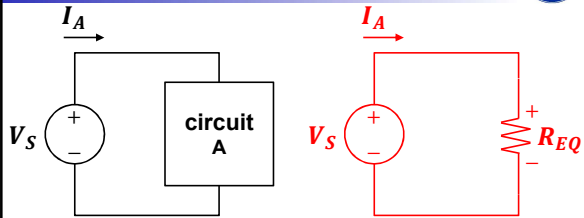


The circuit in red is equivalent to circuit A if

$$R_{EQ} = \frac{V_S}{I_A}$$

Resistors in series



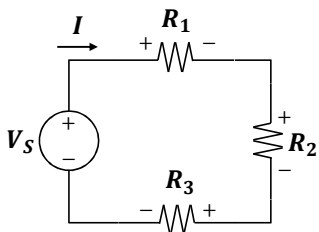
- Two resistors are **in series** if the same current flows from one to another



Resistors in series



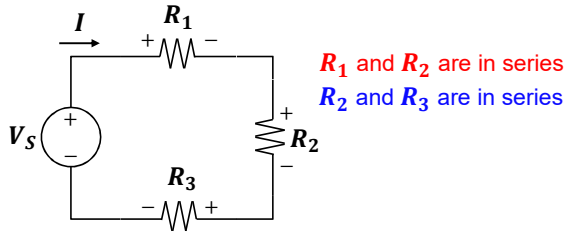
- Two resistors are **in series** if the same current flows from one to another



Resistors in series



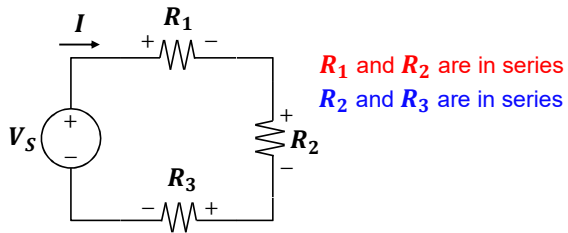
- Two resistors in series always share **one common node**



Resistors in series



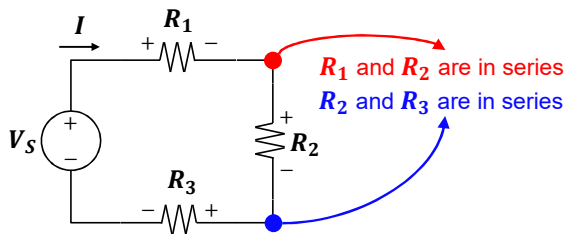
- Two resistors in series always share **one common node**



Resistors in series



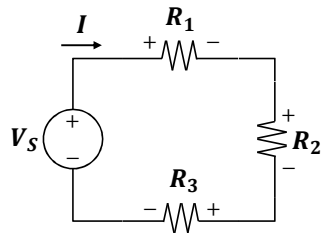- If the same current flows through N distinct resistors then the N resistors are **in series**




R_1 , R_2 , and R_3 are in series

Resistors in series



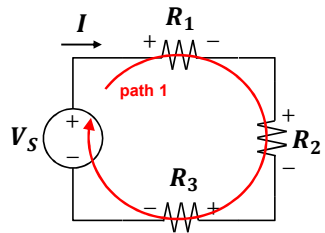- If the same current flows through N distinct resistors then the N resistors are **in series**




KVL at path 1: $R_1 I + R_2 I + R_3 I - V_S = 0$

Resistors in series



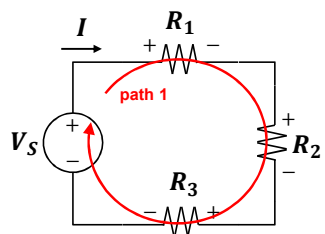- If the same current flows through N distinct resistors then the N resistors are **in series**



$$R_{EQ} = \frac{V_S}{I}$$


$$= R_1 + R_2 + R_3$$

KVL at path 1: $R_1 I + R_2 I + R_3 I - V_S = 0$

Resistors in series



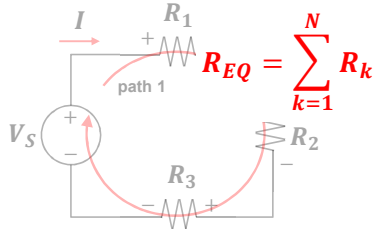N resistors **in series** are equivalent to a single resistor whose resistance R_{EQ} is:




KVL at path 1: $R_1 I + R_2 I + R_3 I - V_S = 0$

Resistors in parallel



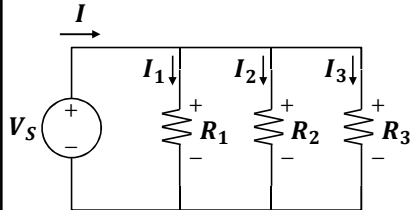
□ Two or more resistors are **in parallel** if the same voltage is across each of them



Resistors in parallel



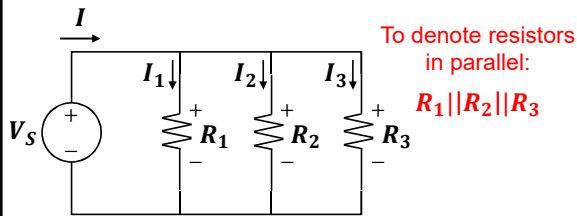□ Two or more resistors are **in parallel** if the same voltage is across each of them




$R_1 I_1 = R_2 I_2 = R_3 I_3 = V_S$

Resistors in parallel



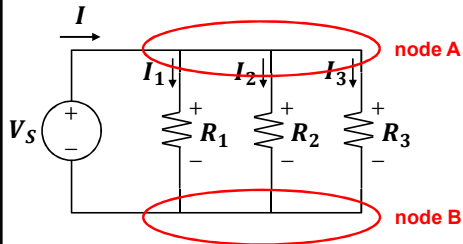
- Resistors in parallel always share **two common nodes**



Resistors in parallel



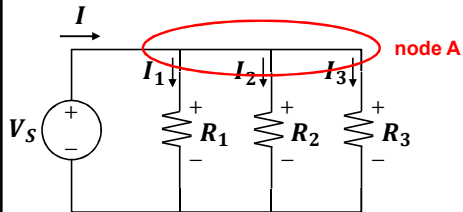- Resistors in parallel always share **two common nodes**




$$\text{KCL at node A: } -I + I_1 + I_2 + I_3 = 0$$

Resistors in parallel



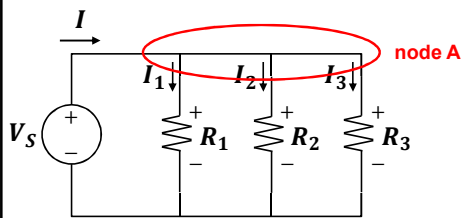- Resistors in parallel always share **two common nodes**




$$\text{KCL at node A: } -I + \frac{V_S}{R_1} + \frac{V_S}{R_2} + \frac{V_S}{R_3} = 0$$

Resistors in parallel



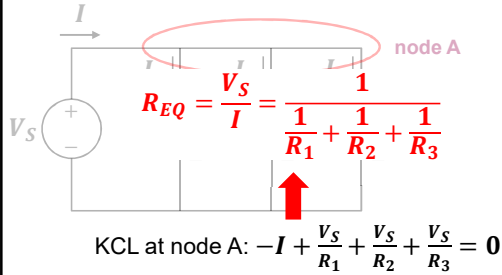
- Resistors in parallel always share **two common nodes**




Resistors in parallel



N resistors **in parallel** are equivalent to a single resistor whose resistance R_{EQ} is:

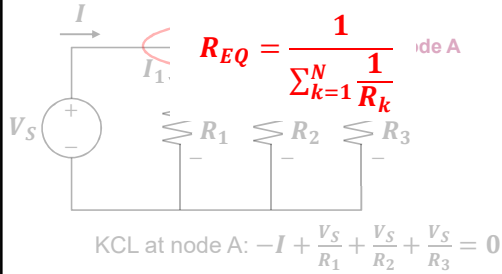


Example 1

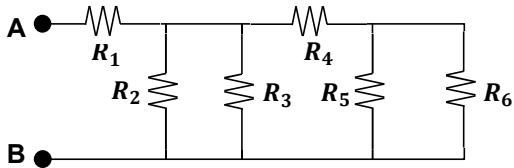

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 3 \Omega$; $R_4 = 1 \Omega$; $R_5 = 4 \Omega$; $R_6 = 12 \Omega$

What is the equivalent circuit resistance between terminals A and B?

Example 1

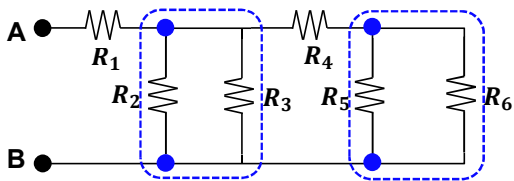


$R_1 = 2 \Omega; R_2 = 6 \Omega; R_3 = 3 \Omega; R_4 = 1 \Omega; R_5 = 4 \Omega; R_6 = 12 \Omega$

$$R_2 || R_3 = 2 \Omega$$

$$R_5 || R_6 = 3 \Omega$$

Example 1

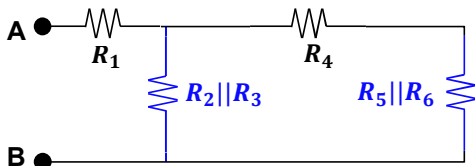


$R_1 = 2 \Omega; R_2 = 6 \Omega; R_3 = 3 \Omega; R_4 = 1 \Omega; R_5 = 4 \Omega; R_6 = 12 \Omega$

$$R_2 || R_3 = 2 \Omega$$

$$R_5 || R_6 = 3 \Omega$$


Example 1

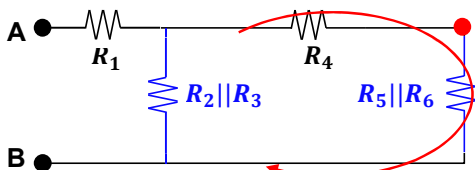

$R_1 = 2 \Omega; R_2 = 6 \Omega; R_3 = 3 \Omega; R_4 = 1 \Omega; R_5 = 4 \Omega; R_6 = 12 \Omega$
 $R_2 || R_3 = 2 \Omega; R_5 || R_6 = 3 \Omega;$

$$R_4 + (R_5 || R_6) = 4 \Omega$$


Example 1

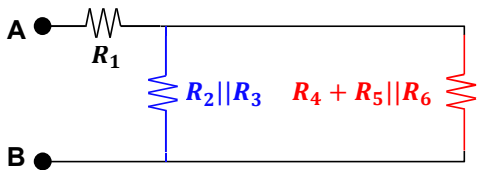

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 3 \Omega$; $R_4 = 1 \Omega$; $R_5 = 4 \Omega$; $R_6 = 12 \Omega$
 $R_2 || R_3 = 2 \Omega$; $R_5 || R_6 = 3 \Omega$;

$$R_4 + (R_5 || R_6) = 4 \Omega$$


Example 1

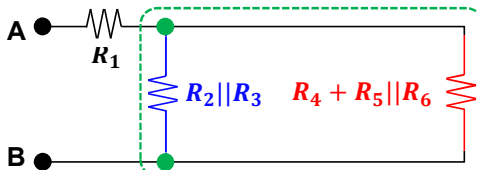

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 3 \Omega$; $R_4 = 1 \Omega$; $R_5 = 4 \Omega$; $R_6 = 12 \Omega$
 $R_2 || R_3 = 2 \Omega$; $R_5 || R_6 = 3 \Omega$; $R_4 + R_5 || R_6 = 4 \Omega$;

$$\tilde{R} = (R_2 || R_3) || (R_4 + (R_5 || R_6)) = 4/3 \Omega$$


Example 1

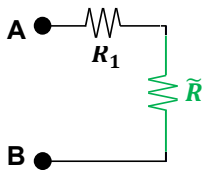

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 3 \Omega$; $R_4 = 1 \Omega$; $R_5 = 4 \Omega$; $R_6 = 12 \Omega$
 $R_2 || R_3 = 2 \Omega$; $R_5 || R_6 = 3 \Omega$; $R_4 + R_5 || R_6 = 4 \Omega$;

$$\tilde{R} = (R_2 || R_3) || (R_4 + (R_5 || R_6)) = 4/3 \Omega$$


Example 1

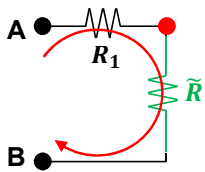

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 3 \Omega$; $R_4 = 1 \Omega$; $R_5 = 4 \Omega$; $R_6 = 12 \Omega$
 $R_2 || R_3 = 2 \Omega$; $R_5 || R_6 = 3 \Omega$; $R_4 + R_5 || R_6 = 4 \Omega$; $\tilde{R} = 4/3 \Omega$;

$$R_{AB} = R_1 + \tilde{R} \cong 3.33 \Omega$$


Example 2

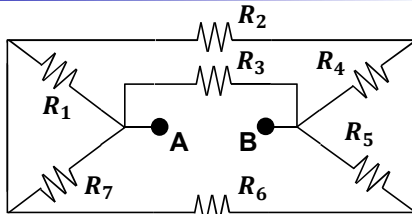

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$

What is the equivalent circuit resistance between terminals A and B?

Example 2

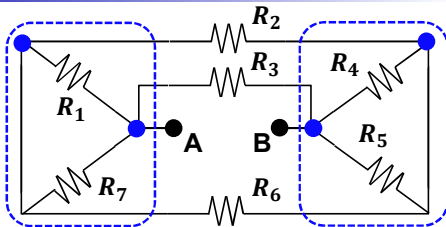


$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$

$$R_1 || R_7 = 1 \Omega$$

$$R_4 || R_5 = 2 \Omega$$

Example 2

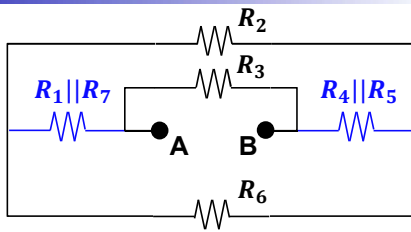


$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$

$$R_1 || R_7 = 1 \Omega$$

$$R_4 || R_5 = 2 \Omega$$


Example 2

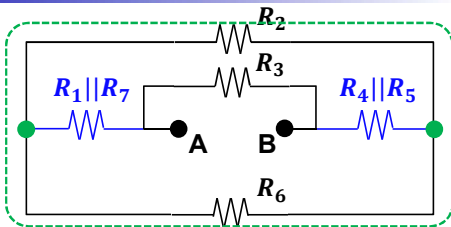

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$; $R_1 || R_7 = 1 \Omega$; $R_4 || R_5 = 2 \Omega$

$$R_2 || R_6 = 3 \Omega$$


Example 2

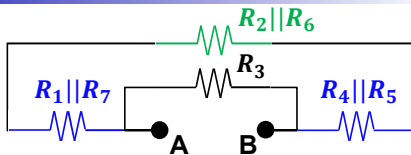

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$; $R_1 || R_7 = 1 \Omega$; $R_4 || R_5 = 2 \Omega$

$$R_2 || R_6 = 3 \Omega$$


Example 2

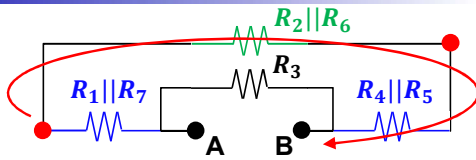

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$; $R_1 || R_7 = 1 \Omega$; $R_4 || R_5 = 2 \Omega$;
 $R_2 || R_6 = 3 \Omega$

$$\tilde{R} = R_1 || R_7 + R_2 || R_6 + R_3 + R_4 || R_5 = 6 \Omega$$


Example 2

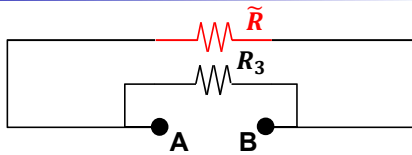

$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$; $R_1 || R_7 = 1 \Omega$; $R_4 || R_5 = 2 \Omega$;
 $R_2 || R_6 = 3 \Omega$

$$\tilde{R} = R_1 || R_7 + R_2 || R_6 + R_3 + R_4 || R_5 = 6 \Omega$$

Example 2

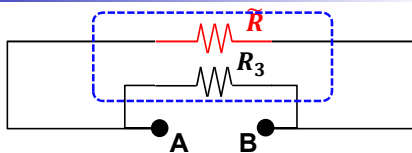


$R_1 = 2 \Omega$; $R_2 = 6 \Omega$; $R_3 = 9 \Omega$; $R_4 = 4 \Omega$; $R_5 = 4 \Omega$;
 $R_6 = 6 \Omega$; $R_7 = 2 \Omega$; $R_1 || R_7 = 1 \Omega$; $R_4 || R_5 = 2 \Omega$;
 $R_2 || R_6 = 3 \Omega$; $\tilde{R} = 6 \Omega$;

$$R_{AB} = \tilde{R} || R_3 = 3.6 \Omega$$

Voltage divider rule



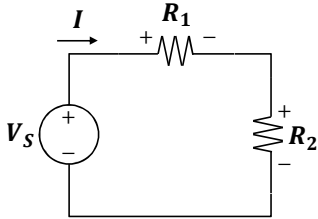
- It allows to calculate the voltage across any individual resistor connected in a series of resistors



Voltage divider rule



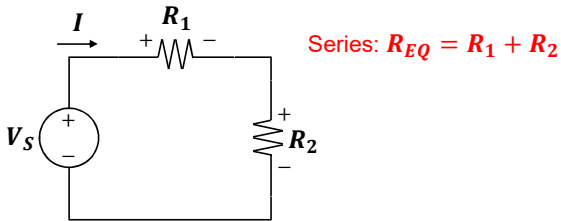
- It allows to calculate the voltage across any individual resistor connected in a series of resistors



Voltage divider rule



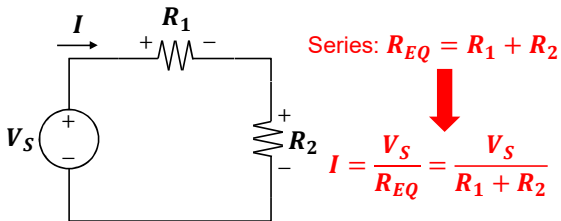- It allows to calculate the voltage across any individual resistor connected in a series of resistors



Voltage divider rule

$$I = \frac{V_S}{R_{EQ}} = \frac{V_S}{R_1 + R_2}$$

$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V_S$$

$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V_S$$

Voltage divider rule

□ The voltage drop across each resistor in a series is a fraction of the original voltage across the entire series

$$V_1 = R_1 I = \frac{R_1}{R_1 + R_2} V_S$$

$$V_2 = R_2 I = \frac{R_2}{R_1 + R_2} V_S$$

Voltage divider rule (VDR)

□ If N resistors are in series (R_1, R_2, \dots, R_N) and the voltage across the series is V_S , the voltage drop across each resistor is:


$$V_k = \frac{R_k}{R_1 + R_2 + \dots + R_N} V_S$$

$k = 1, 2, 3, \dots, N$

Current divider rule



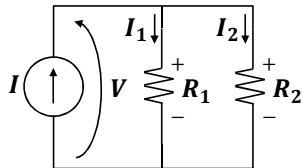
- It allows to calculate the current through any resistor connected in parallel resistor circuits



Current divider rule



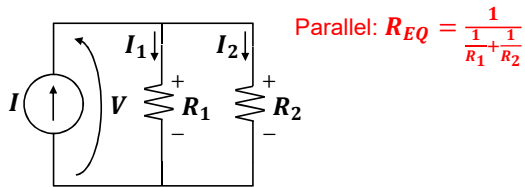
- It allows to calculate the current through any resistor connected in parallel resistor circuits



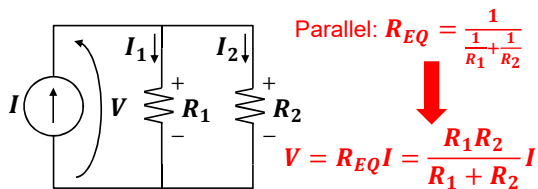
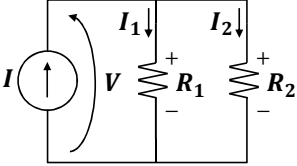
Current divider rule



- It allows to calculate the current through any resistor connected in parallel resistor circuits




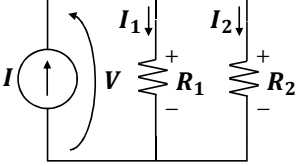
Current divider rule 

$$V = R_{EQ}I = \frac{R_1 R_2}{R_1 + R_2} I$$


$$I_1 = \frac{V}{R_1} = \frac{R_2}{R_1 + R_2} I$$


$$I_2 = \frac{V}{R_2} = \frac{R_1}{R_1 + R_2} I$$

Current divider rule 


$$V = R_{EQ}I = \frac{R_1 R_2}{R_1 + R_2} I$$


$$I_1 = \frac{V}{R_1} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

$$I_2 = \frac{V}{R_2} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

Current divider rule 

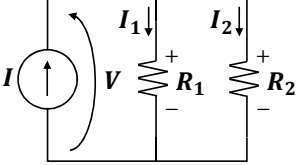□ The current through each resistor in a parallel circuit is a fraction of the original current and depends on the resistance



$$I_1 = \frac{V}{R_1} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

$$I_2 = \frac{V}{R_2} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

Current divider rule (CDR)




- If N resistors are in parallel (R_1, \dots, R_N) and the current entering (leaving) the common nodes is I , then the current through each resistor is:

$$I_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} I$$

$k = 1, 2, 3, \dots, N$


Example 3

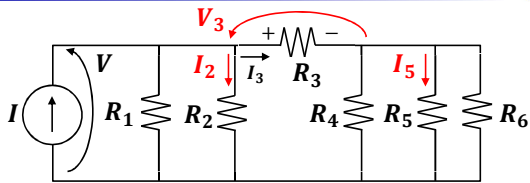

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$

What is the value of I_2 , I_5 , and V_3 ?


Example 3

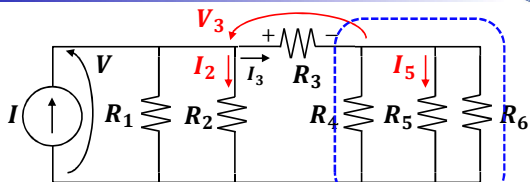

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$

$$\tilde{R}_a = R_4 \parallel R_5 \parallel R_6 = 4 \Omega$$


Example 3

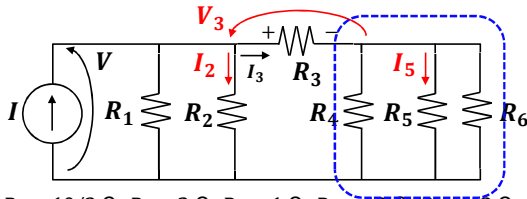

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$


$$\text{CDR: } I_5 = \frac{\frac{1}{R_5}}{\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}} I_3 = \frac{1}{3} I_3$$

Example 3

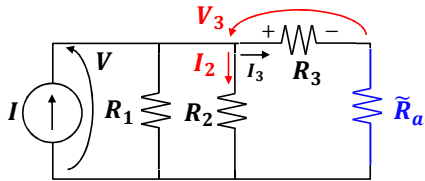

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$


Example 3

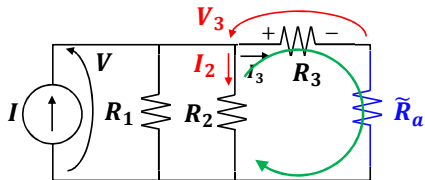

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$

$$\tilde{R}_b = R_3 + \tilde{R}_a = 5 \Omega$$


Example 3

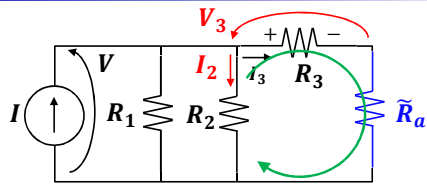

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$; $\tilde{R}_b = 5 \Omega$

$$\text{VDR: } V_3 = \frac{R_3}{R_3 + \tilde{R}_a} V$$


Example 3

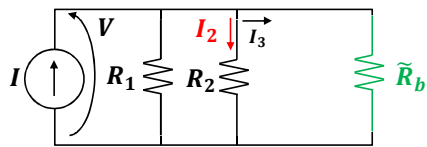

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$; $\tilde{R}_b = 5 \Omega$

$$\text{CDR: } I_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_b}} I = 0.5I = 2.5 \text{ A}$$


Example 3

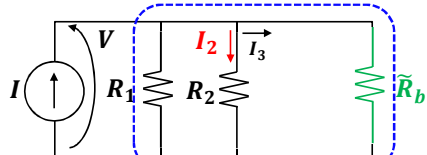

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\tilde{R}_a = 4 \Omega$; $\tilde{R}_b = 5 \Omega$

$$\text{CDR: } I_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_b}} I = 0.5I = 2.5 \text{ A}$$


Example 3

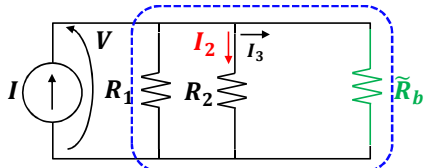

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\bar{R}_a = 4 \Omega$; $\bar{R}_b = 5 \Omega$

$$\text{CDR: } I_3 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_b}} I = 0.2I = 1.0 \text{ A}$$


Example 3

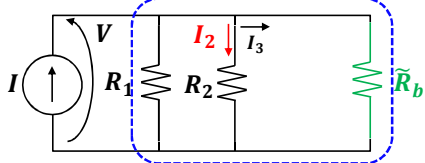

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\bar{R}_a = 4 \Omega$; $\bar{R}_b = 5 \Omega$

$$\text{CDR: } I_5 = \frac{1}{3} I_3 \cong 0.3 \text{ A}$$

Example 3

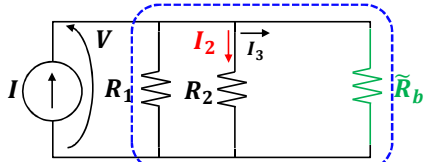

$R_1 = 10/3 \Omega$; $R_2 = 2 \Omega$; $R_3 = 1 \Omega$; $R_4 = 12 \Omega$; $R_5 = 12 \Omega$;
 $R_6 = 12 \Omega$; $I = 5 \text{ A}$; $\bar{R}_a = 4 \Omega$; $\bar{R}_b = 5 \Omega$

$$\text{VDR: } V_3 = \frac{R_3}{R_3 + \bar{R}_a} V = \frac{R_3}{R_3 + \bar{R}_a} R_2 I_2 = 1.0 \text{ V}$$
